

AMPLIFIER DESIGNING

PURPOSE OF DESIGN:-

For amplifying human voice signals to make others hear clearly while wearing face masks.

FREQUENCY RESPONSE RANGE:- 20Hz -20kHz

POWER OUTPUT REQUIRED:- 12 Watts

SPECIFICATION OF MICROPHONE AND LOUDSPEAKER:-

MICROPHONE

- Microphone 9*7mm
- Model name - SKU: 699586
- Frequency Range: 50 – 20KHz
- Microphone sensitivity 56 – 58DB
- Low noise
- Low power consumption

SPEAKER

- Power Rating - 6W
- Impedance - $8 \pm 15\%$
- Output SPL - 95 ± 3 dBA
- Frequency Range- 230–12000 Hz

PART NUMBER OF TRANSISTOR USED:- 2N3904

CALCULATIONS:-

Calculations

* Mid band frequency gain = 50

* Transistor used \rightarrow 2N3464

* Maximum Rating :- $V_{DS} = 60V$ $V_{CE} = 40V$ $V_{EB} = 6V$
 $I_C = 200mA$

* Nominal Rating :- $V_{CE} = 1V$ $I_C = 10mA$ $h_{FE} = 100-300$

* Output Swing = 10V

$$\rightarrow V_{CC} = 12V \quad V_{CE} = 6V \\ V_{RE} = 4.8V \quad V_{RE} = 1.2V$$

$$\rightarrow \text{Design of } R_C \Rightarrow V_{RC} = I_C R_C \\ R_C = \frac{4.8}{10mA} = \underline{\underline{480\Omega}}$$

$$\rightarrow \text{Design of } R_E \Rightarrow V_{RE} = I_E R_E \\ R_E = \frac{1.2}{10mA} = \underline{\underline{120\Omega}}$$

$$\rightarrow \text{Design of } R_2 \Rightarrow I_B = 100\mu A \\ V_{R2} = \beta I_B R_2 = .6 + 1.2$$

$$\rightarrow \text{Design of } R_1 \Rightarrow R_2 = \frac{1.8}{9 \times 100\mu A} = \underline{\underline{2k\Omega}} \\ V_{R1} = V_{CC} - V_{R2} = 12 - 1.8 = 10.2V$$

$$R_1 = \frac{10.2}{10 \times 10\mu A}$$

$$\rightarrow \text{Design of } R_L \Rightarrow \underline{\underline{10.2k\Omega}}$$

$$50 = \frac{R_L \times 480}{R_L + 480} \quad R_L = \underline{\underline{169\Omega}}$$
$$\frac{50(R_L + 480)}{2.5} = R_L \times 480$$

$$\frac{1}{R_i} = \frac{1}{2 \times 10^3} + \frac{1}{10.2 \times 10^3} + \frac{1}{252.5}$$

$$R_i = \underline{219 \Omega}$$


→ Let lower cutoff frequency = 50 Hz

$$C_{C1} = C_{C2} = \frac{1}{2\pi \times 219 \times 50} = \underline{14 \mu F}$$

$$C_E = \frac{1}{2\pi \times 50 \times 12} = \underline{265 \mu F}$$

$$X_{CE} = \frac{V_E}{10}$$

DESIGN:-

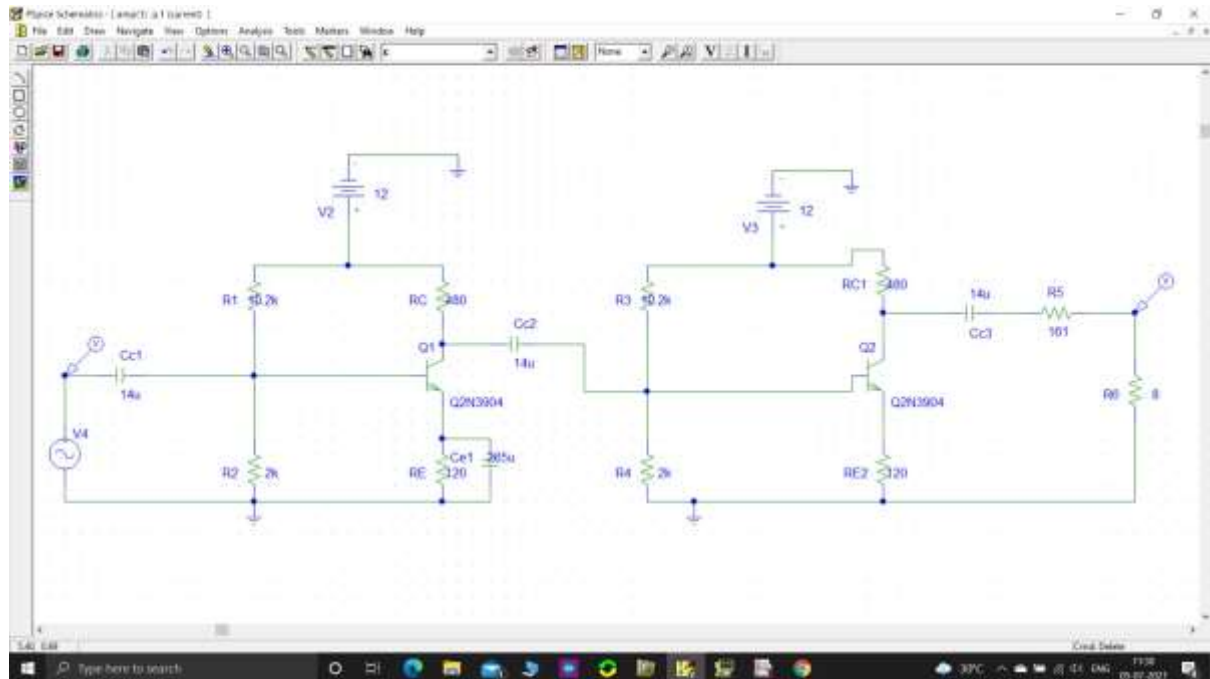

OUTPUT:-



FREQUENCY RESPONSE:-

